

基于FPGA的 时序逻辑电路设计和实现 EDA实验二

赵晓燕
电工电子实验中心

主要内容

- 一. 基本语法
- 二. `always`模块
- 三. 时序电路的HDL描述
- 四. 阻塞式与非阻塞式赋值
- 五. 有限状态机的HDL描述
- 六. EDA实验二内容

基本语法-----数据类型

常量

- 数字

`8'b0000_0100`

`6'h1f`

`128`

- 参数

`parameter WIDTH = 8;`

`wire [WIDTH-1:0] data;`

`4'b10_11`



下划线 (可以忽略)

进制 (d,b,o,h)

位宽 (十进制数表示)

变量

- 线型 (wire) assign赋值 =
- 寄存器型 (reg) always赋值 <=

基本语法-----运算符

关系运算符 (>、<、>=、<=、==、!=)

- `(4'b1011 < 4'b0111) = 0`
- `(4'b1011 != 4'b0111) = 1`

条件运算符(?:)

`<conditional_expression> ? <expression1> : <expression2>`

- `assign out=(sel)?in1:in0;`

级联运算符 {}

- 级联多个运算数
`{5'b10110, 2'b10, 1'b0}=8'b1011_0100`
- 同一个运算数级联多次
`{3{3'b101}}=9'b101_101_101`

基本语法----运算符

位运算符 \sim 、 $\&$ 、 $|$ 、 \wedge 、 $\sim\wedge$ (异或)

- 运算数是矢量，运算逐位进行

```
4'b0100 | 4'b1001 = 4'b1101  
~8'b0110_1100 = 8'b1001_0011
```

$\sim a$	NOT
$a \& b$	AND
$a b$	OR
$a \wedge b$	XOR
$a \sim\wedge b$	XNOR

逻辑运算符 $!$ 、 $\&\&$ 、 $||$

- 产生一个逻辑值

```
4'b0000 || 4'b0111 = 1  
4'b0000 && 4'b0111 = 0  
!4'b0000 = 1
```

$!a$	NOT
$a \&\& b$	AND
$a b$	OR

基本语法-----运算符

算数运算符 (+、-、*、/、%)

- /、% (模运算) 运算符当右边运算数是2的幂次方时可综合

移位运算符 (>>、<<)

`8'b0011_1100 >> 2 = 8'b0000_1111`

`8'b0011_1100 << 2 = 8'b1111_0000`

<code>&a</code>	AND
<code>~&</code>	NAND
<code> </code>	OR
<code>~ </code>	NOR
<code>^</code>	XOR

位缩减运算符 & ~& | ~| ^ ^~

- 只有一个运算数
- 对每个向量完成逐位运算
- 产生1比特运算结果

`&4'b0101 = 0 & 1 & 0 & 1 = 0`

`|4'b0101 = 0 | 1 | 0 | 1 = 1`


模块定义

```
module adder( A, B, cout, sum );  
    input  [3:0] A, B;  
    output          cout;  
    output [3:0] sum;
```

1995版

```
// HDL modeling of  
// adder functionality
```

```
endmodule
```

 




```
module adder( input  [3:0] A, B,  
              output          cout,  
              output [3:0] sum );
```

```
// HDL modeling of 4 bit  
// adder functionality
```

```
endmodule
```

2001版

模块实例化

   

```
module adder( input  [3:0] A, B,  
              output          cout,  
              output [3:0] S );
```

```
FA fa0( ... );  
FA fa1( ... );  
FA fa2( ... );  
FA fa3( ... );
```


```
endmodule
```

```
module FA( input  a, b, cin  
          output cout, sum );
```

```
// HDL modeling of 1 bit  
// adder functionality
```

```
endmodule
```


模块连接

 

```
module adder( input  [3:0] A, B,
               output      cout,
               output [3:0] S );

  wire c0, c1, c2;

  FA fa0( A[0], B[0], 0, c0, S[0] );
  FA fa1( A[1], B[1], c0, c1, S[1] );
  FA fa2( A[2], B[2], c1, c2, S[2] );
  FA fa3( A[3], B[3], c2, cout, S[3] );

endmodule
```

- 定义模块间连线 **wire**
- 端口连接可通过变量位置或名字

```
FA fa0( .a(A[0]), .b(B[0]),
        .cin(0), .cout(c0),
        .sum(S[0] ) );

FA fa1( .a(A[1]), .b(B[1]),
        ...
```


always 模块表达形式

always@ (敏感列表)
赋值语句

- **always@ (a, b, c)**
- **always@ (*)**
- **always@ (posedge clk)**
- **always@ (negedge clk, posedge rst)**

always 模块使用

- 时序always模块：always@(posedge clock) 用<=赋值；
- 组合always模块：always@ (*) 用=赋值；
- always模块中的变量必须声明为reg型；
- 一个always模块中不能混用<=, =赋值；
- 等价语句
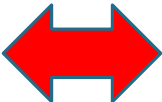
```
reg z
always@ (*)  assign z=x&&y
z=x&&y
```

组合always模块

```
module mux4( input  a, b, c, d,  
             input [1:0] sel,  
             output reg out );
```

```
    always @( * )  
    begin  
        case ( sel )  
            0 : out = a;  
            1 : out = b;  
            2 : out = c;  
            3 : out = d;  
        endcase  
    end
```

```
endmodule
```


- always语句块可以包含：
if else语句、case语句、for、
while循环语句
- 一般每个if 语句要与else匹配
- case语句分支要完整，否则要包括default

8位二选一数据选择器

```
module Mux_2to1_8bit(  
    input  wire[7:0] in0,  
    input  wire[7:0] in1,  
    input  wire      sel,  
    output wire [7:0] out  
);  
  
    assign out=(sel)?in1:in0;  
  
endmodule
```

```
output  reg [7:0]  out  
always@(*)  
    case (sel)  
        1'b0:  out=in0;  
        1'b1:  out=in1;  
    endcase
```
 
```
output  reg [7:0]  out  
always@(*)  
    if (sel==0)  
        out=in0;  
    else  
        out=in1;
```



分支不完全的case语句

```
module mux4(input a, b, c,  
            input [1:0] sel,  
            output reg out );
```

```
always @( a or b or c or sel )  
begin
```

```
    case ( sel )
```

```
        2'b00 : out = a;
```



```
        2'b01 : out = b;
```

```
        2'b10 : out = c;
```

```
    endcase
```

```
end
```


```
endmodule
```

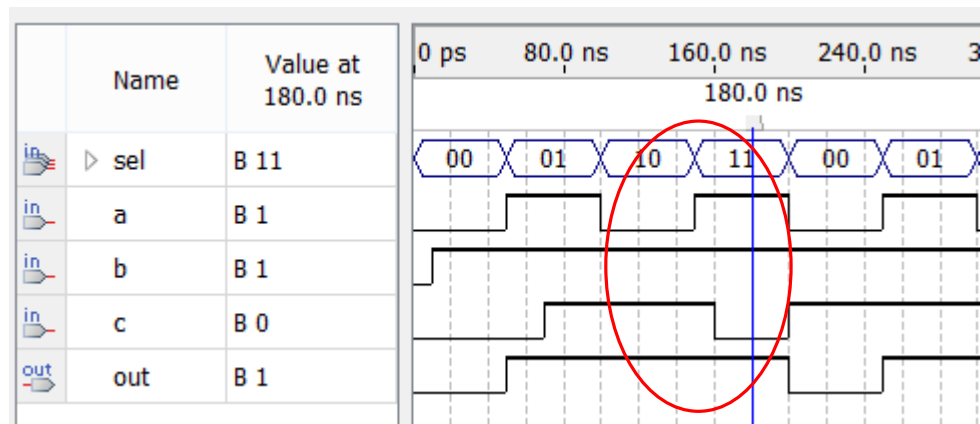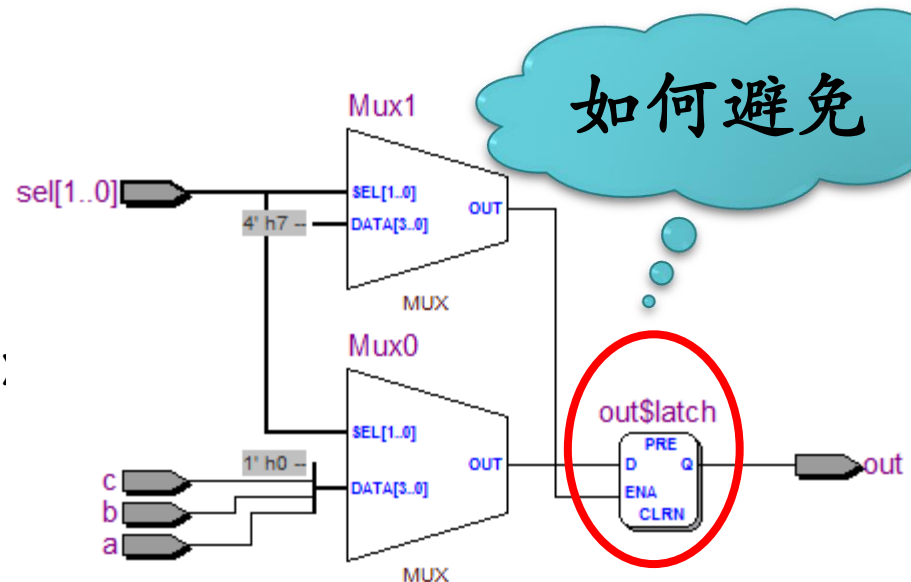

分支不完全的case语句

```
always @( a or b or c or sel
)
begin
  case ( sel )
    2'b00 : out = a;
    2'b01 : out = b;
    2'b10 : out = c;
    default: out=1'bx;
  endcase
end
```
 
```
always @( a or b or c or sel
)
begin
  out=1'bx;
  case ( sel )
    2'b00 : out = a;
    2'b01 : out = b;
    2'b10 : out = c;
  endcase
end
```




组合与时序always 模块

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

 
    always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



时序电路-----D触发器

```
module latc1
(input clk,
 input d,
 output reg q);
always @(clk or d )
begin
    if (clk)
        q<=d;
    end
endmodule
```


电平触发

 

D型锁存器


```
module FF0
(input clk,
 input d,
 output reg q);
always @(posedge clk )
begin
    q<=d;
end
endmodule
```

边沿触发

 


时序电路-----D触发器
 
```
module FF0(input clk,input
d,output reg q);
always @( posedge clk )
begin
    q<=d;
end
endmodule
```


 
```
module FF0(input clk,input
d,output reg q);
always @( posedge clk )
begin
    if (en)
    q<=d;
end
endmodule
```



时序电路-----D触发器

```
module FF1#(parameter WIDTH=1)
  (input clk,
   input [WIDTH-1:0]d,
   input en,
   output reg [WIDTH-1:0] q);
  always @(posedge clk)
  begin
    if(en)
      q<=d;
    end
  endmodule
```

parameter修
改电路参数

时序电路-----D触发器

```
always @( posedge clk )  
begin  
    if (~resetN)  
        Q<=0;  
    else if (enble)  
        Q<=D;//同步置数  
end
```

同步复位

```
always @( posedge clk or negedge resetN )  
begin  
    if (~resetN)  
        Q<=0;  
    else if (enble)  
        Q<=D;//同步置数  
end
```

异步复位

时序电路-----D触发器

```
module flipflop
(input clk,resetN,set,
input [1:0]D,din,
output reg [1:0]q);
```

```
always @(posedge clk or negedge resetN or posedge set)
begin
```

```
    if (~resetN)
        q<=0;
```



```
    else if (set)
        q<=D; //
```

异步置数

```
    else q<=din;
```

```
end
```

```
endmodule
```

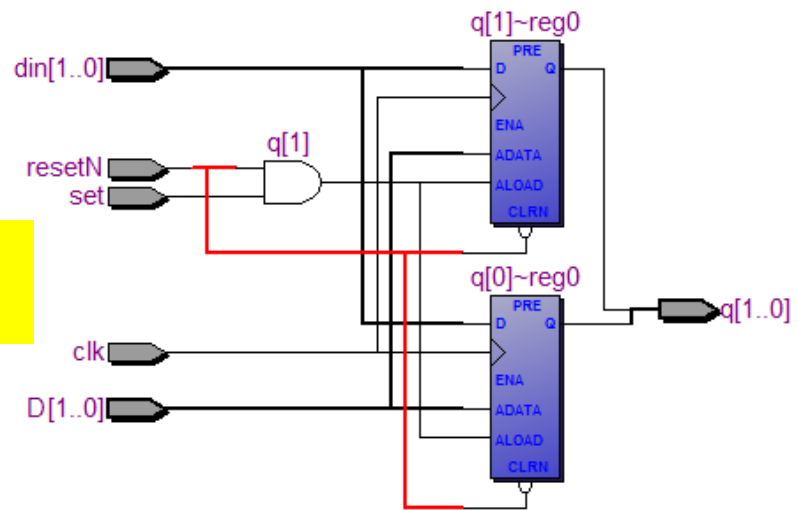 

时序电路-----计数器

```
module dff_asyn3(clk,d,rst,en,q);  
input clk,rst,en;  
input [1:0]d;  
output [1:0]q;  
reg [1:0]q;  
  
always@(posedge clk or negedge rst)  
begin  
    if(!rst)  
        q<=0; // 异步清零  
    else if(!en)  
  
        q<=d; // 同步置数  
    else  
        q<=q+1; // 计数  
  
end  
endmodule
```

计数

■ Behavioral description of the '163 counter:

```
module counter(LDbar, CLRbar, P, T, CLK, D,  
              count, RCO);  
    input LDbar, CLRbar, P, T, CLK;  
    input [3:0] D;  
    output [3:0] count;  
    output RCO;  
    reg [3:0] Q;
```

```
    always @ (posedge CLK) begin
```

```
        if (!CLRbar) Q <= 4'b0000;  
        else if (!LDbar) Q <= D;  
        else if (P && T) Q <= Q + 1;
```


```
    end
```

```
    assign count = Q;
```

```
    assign RCO = Q[3] & Q[2] & Q[1] & Q[0] & T;
```

```
endmodule
```


**priority logic for
control signals**

 

**RCO gated
by T input**

时序电路-----分频器

```
module femp(clki,rst,clk1,clk2);  
input clki,rst;  
output clk1,clk2;  
  
reg [30:0]q;  
  
always@(posedge clki, negedge rst)  
  
    if(!rst)    q<=0;  
    else    q=q+1;  
  
assign clk1=q[16]; //输出250hz  
assign clk2=q[24]; //输出1HZ  
  
endmodule
```



计数器输出
相邻位满足
2倍频关系

时序电路-----分频器

```
module femp(clk,rst,en,count);  
input clk,rst;  
output en;  
output [3:0] count;  
reg [3:0] count;
```

```
always@(posedge clk,negedge rst)  
begin
```

```
    if (!rst) count<=0;
```


```
        else count<=(count==4)?0:count+1;
```

```
end
```

```
assign en=(count==4);
```

```
endmodule
```


产生使能
控制信号

 

非阻塞 (\leq) 和阻塞赋值 ($=$)


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out simultaneously receive the old values of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 “At each rising clock edge, $q1 = in$.
After that, $q2 = q1 = in$.
After that, $out = q2 = q1 = in$.
Therefore $out = in$.”



移位寄存器

非阻塞 (\leq) 和阻塞赋值 ($=$)

■ 阻塞式赋值

```
always @(a,b) begin
```

```
  x=a;
```

```
  y=b&x;
```

```
  z=x|y;
```

```
end
```

a	b	x	y	z
0	0	0	0	0
1	1	1	1	1

■ 非阻塞式赋值

```
always @(a,b) begin
```

```
  x<=a;
```

```
  y<=b&x;
```

```
  z<=x|y;
```

```
end
```

a	b	x	y	z
0	0	0	0	0
1	1	1	0	0

- 阻塞赋值 ($=$)，数据计算与更新同时进行
- 非阻塞赋值 (\leq)，先进行数据计算，所有赋值语句执行完，再进行数据更新。

Coding Guidelines


The following helpful guidelines are from the Cummings paper. If followed, they ensure your simulation results will match what they synthesized hardware will do:

1. When modeling sequential logic, use nonblocking assignments.
2. When modeling latches, use nonblocking assignments.
3. When modeling combinational logic with an always block, use blocking assignments.
4. When modeling both sequential and "combinational" logic within the same always block, use nonblocking assignments.
5. Do not mix blocking and nonblocking assignments in the same always block.
6. Do not make assignments to the same variable from more than one always block.
7. Use \$strobe to display values that have been assigned using nonblocking assignments.
8. Do not make assignments using #0 delays.

For more info see: http://www.sunburst-design.com/papers/CummingsSNUG2002Boston_NBAwithDelays.pdf

时序电路-----有限状态机FSM

 
- Finite State Machines (FSMs) are a useful abstraction for sequential circuits with centralized “states” of operation
- At each clock edge, combinational logic computes *outputs* and *next state* as a function of *inputs* and *present state*




Two Types of FSMs

Moore and Mealy FSMs : different output generation

- Moore FSM:

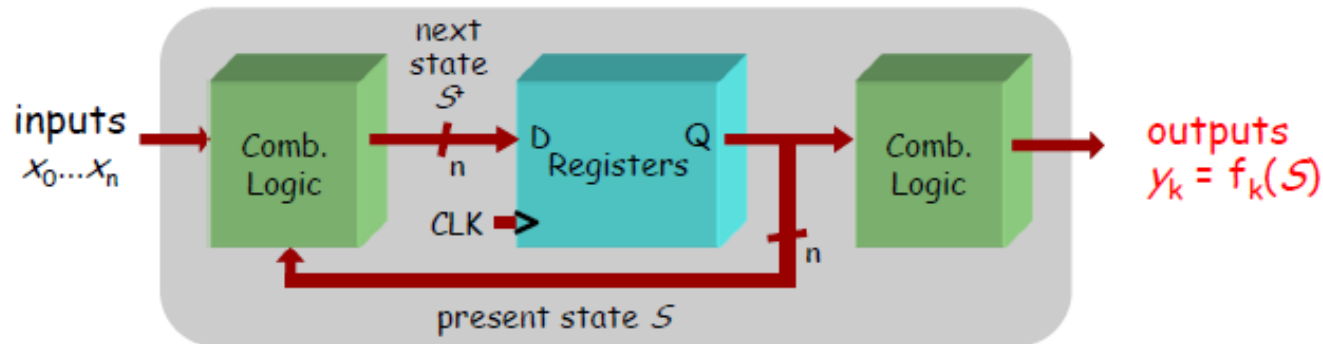


- Mealy FSM:

 


有限状态机FSM设计

Step 1: State Transition Diagram

- Block diagram of desired system:

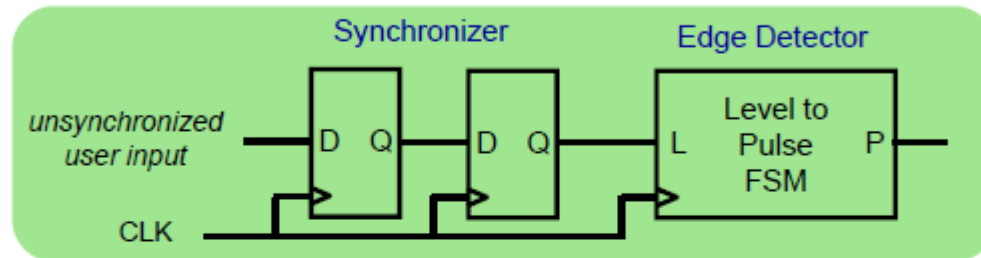


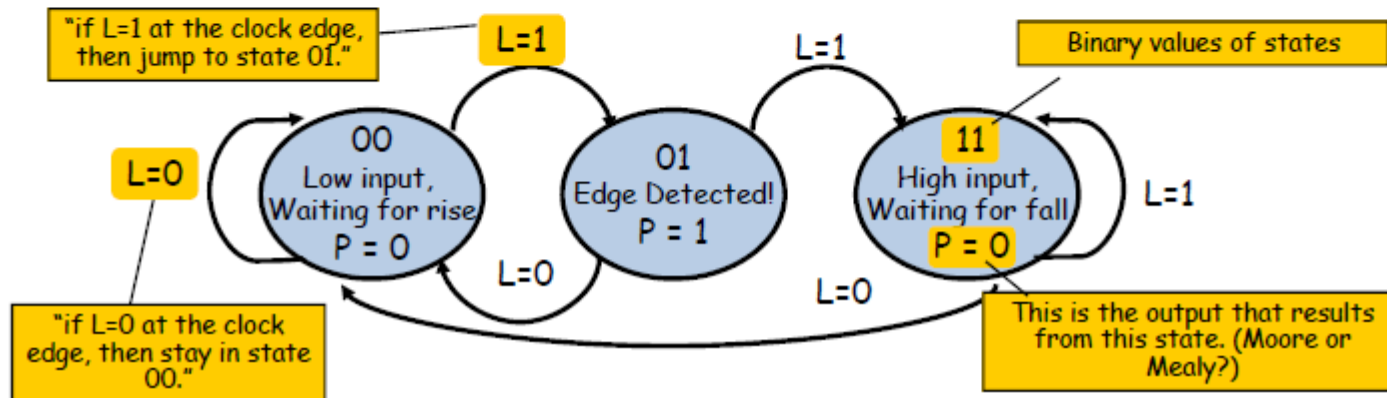- State transition diagram is a useful FSM representation and design aid:




Step 2: Logic Derivation

 Transition diagram is readily converted to a state transition table (just a truth table)




Current State		In	Next State		Out
S_1	S_0	L	S_1^+	S_0^+	P
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	1
1	1	0	0	0	0
1	1	1	1	1	0

 
- Combinational logic may be derived using Karnaugh maps




Moore Level-to-Pulse Converter

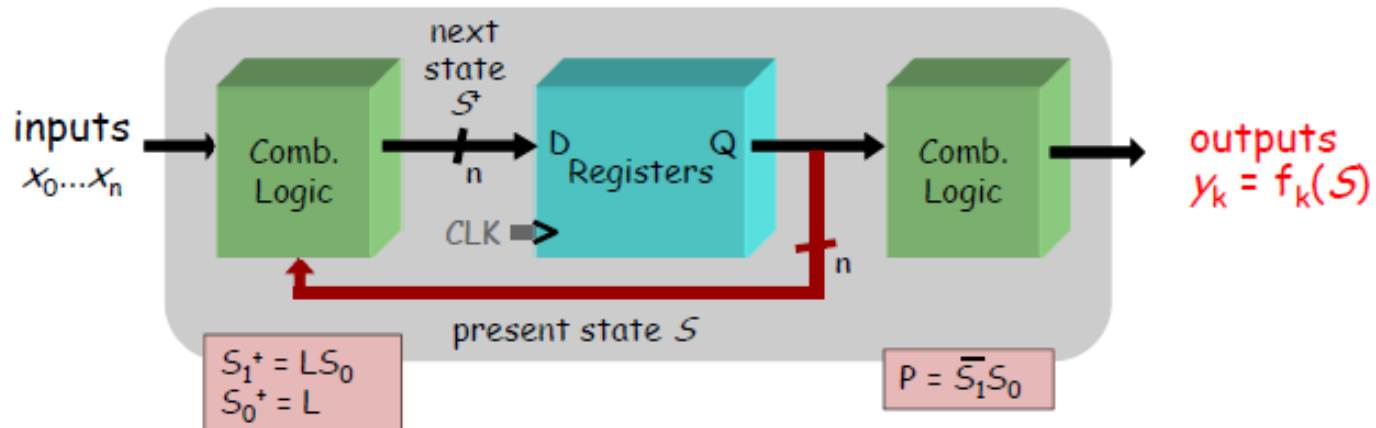

 Moore FSM circuit implementation of level-to-pulse converter:



两段式FSM（输出组合电路）

 

*FSMs are easy in Verilog.
Simply write one of each:*

- State register
(sequential always block)
- Next-state combinational logic
(comb. always block with case)
- Output combinational logic block
(comb. always block *or* assign statements)

```
module mooreVender (  
    input N, D, Q, clk, reset,  
    output DC, DN, DD,  
    output reg [3:0] state);  
  
    reg next;
```

States defined with **parameter** keyword

```
parameter IDLE = 0;  
parameter GOT_5c = 1;  
parameter GOT_10c = 2;  
parameter GOT_15c = 3;  
parameter GOT_20c = 4;  
parameter GOT_25c = 5;  
parameter GOT_30c = 6;  
parameter GOT_35c = 7;  
parameter GOT_40c = 8;  
parameter GOT_45c = 9;  
parameter GOT_50c = 10;  
parameter RETURN_20c = 11;  
parameter RETURN_15c = 12;  
parameter RETURN_10c = 13;  
parameter RETURN_5c = 14;
```

State register defined with sequential
always block

```
always @ (posedge clk or negedge reset)  
    if (!reset) state <= IDLE;  
    else state <= next;
```

两段式FSM（输出组合电路）

Next-state logic within a combinational **always** block

```
always @ (state or N or D or Q) begin
    case (state)
        IDLE:      if (Q) next = GOT_25c;
                   else if (D) next = GOT_10c;
                   else if (N) next = GOT_5c;
                   else next = IDLE;

        GOT_5c:    if (Q) next = GOT_30c;
                   else if (D) next = GOT_15c;
                   else if (N) next = GOT_10c;
                   else next = GOT_5c;

        GOT_10c:   if (Q) next = GOT_35c;
                   else if (D) next = GOT_20c;
                   else if (N) next = GOT_15c;
                   else next = GOT_10c;

        GOT_15c:   if (Q) next = GOT_40c;
                   else if (D) next = GOT_25c;
                   else if (N) next = GOT_20c;
                   else next = GOT_15c;

        GOT_20c:   if (Q) next = GOT_45c;
                   else if (D) next = GOT_30c;
                   else if (N) next = GOT_25c;
                   else next = GOT_20c;
```

```
GOT_25c:  if (Q) next = GOT_50c;
           else if (D) next = GOT_35c;
           else if (N) next = GOT_30c;
           else next = GOT_25c;
```

```
GOT_30c:  next = IDLE;
GOT_35c:  next = RETURN_5c;
GOT_40c:  next = RETURN_10c;
GOT_45c:  next = RETURN_15c;
GOT_50c:  next = RETURN_20c;

RETURN_20c: next = RETURN_10c;
RETURN_15c: next = RETURN_5c;
RETURN_10c: next = IDLE;
RETURN_5c:  next = IDLE;
```

```
default: next = IDLE;
endcase
end
```

Combinational output assignment


```
assign DC = (state == GOT_30c || state == GOT_35c ||
             state == GOT_40c || state == GOT_45c ||
             state == GOT_50c);
assign DN = (state == RETURN_5c);
assign DD = (state == RETURN_20c || state == RETURN_15c ||
             state == RETURN_10c);

endmodule
```


FSM Output Glitching

- FSM state bits may not transition at precisely the same time
- Combinational logic for outputs may contain hazards
- Result: your FSM outputs may glitch!


during this state transition...

 

 ...the state registers may transition like this...




 ...causing the DC output to **glitch** like this!



```
assign DC = (state == GOT_30c || state == GOT_35c ||  
             state == GOT_40c || state == GOT_45c ||  
             state == GOT_50c);
```

三段式FSM（输出寄存器电路）

 



- Move output generation into the sequential always block
- Calculate outputs based on next state
- Delays outputs by one clock cycle. Problematic in some application.

```
reg DC,DN,DD;



// Sequential always block for state assignment
always @ (posedge clk or negedge reset) begin
    if (!reset) state <= IDLE;
    else if (clk) state <= next;

    DC <= (next == GOT_30c || next == GOT_35c ||
           next == GOT_40c || next == GOT_45c ||
           next == GOT_50c);
    DN <= (next == RETURN_5c);
    DD <= (next == RETURN_20c || next == RETURN_15c ||
           next == RETURN_10c);
end
```

状态图

 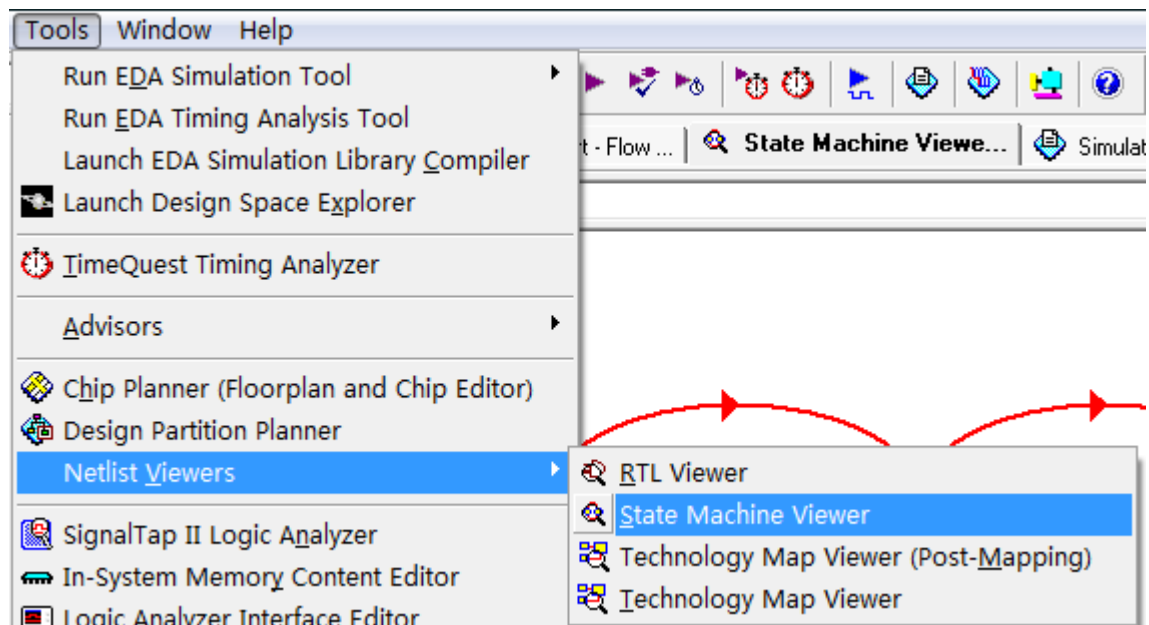

电路结构图

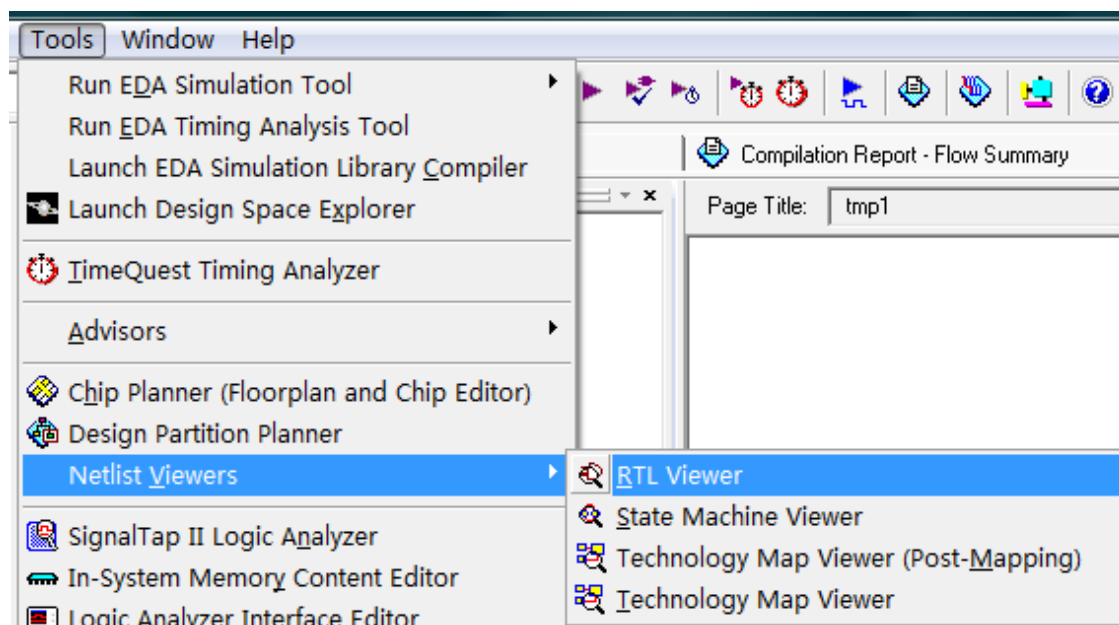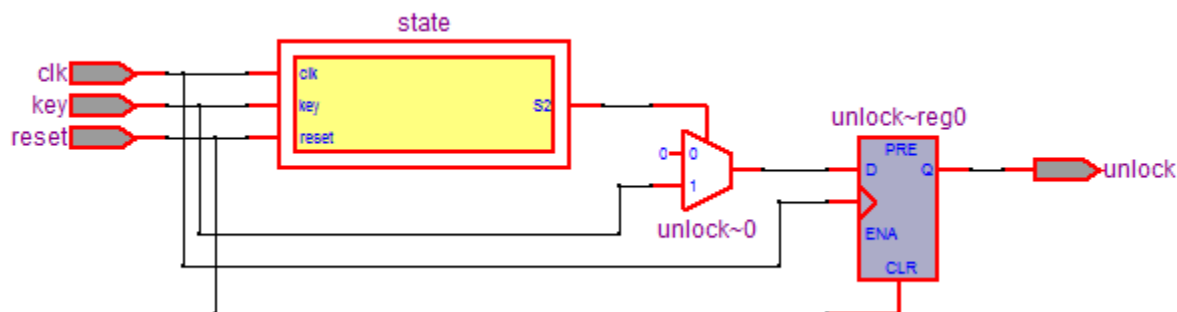




EDA实验二内容


Vending machine

利用实验板上的拨码开关和按键开关模拟**投币**、**购物**和**退币**输入，用**发光二极管**模拟各种提示信息，用**数码管**显示余额，实现一个自动售货机内部控制电路。要求满足如下规格：


 
- 1) 可接受**5角**、**1元**和**5元**的投币，每次购买允许投入多种不同币值的钱币；用**3只数码管**显示当前投币金额，如055表示已投币5.5元；
- 2) 可售出价格分别为**1.5元**和**2.5元**的商品，假设用户每次购买时只选择单件、一种商品；允许用户多次购买商品，每次购买后，可以进行补充投币；
- 3) 选择购买商品后，如果投币**金额不足**，则提醒；否则，售出相应的商品，并提醒用户取走商品；
- 4) 若用户选择**退币**，则退回余下的钱，并提醒用户取钱。



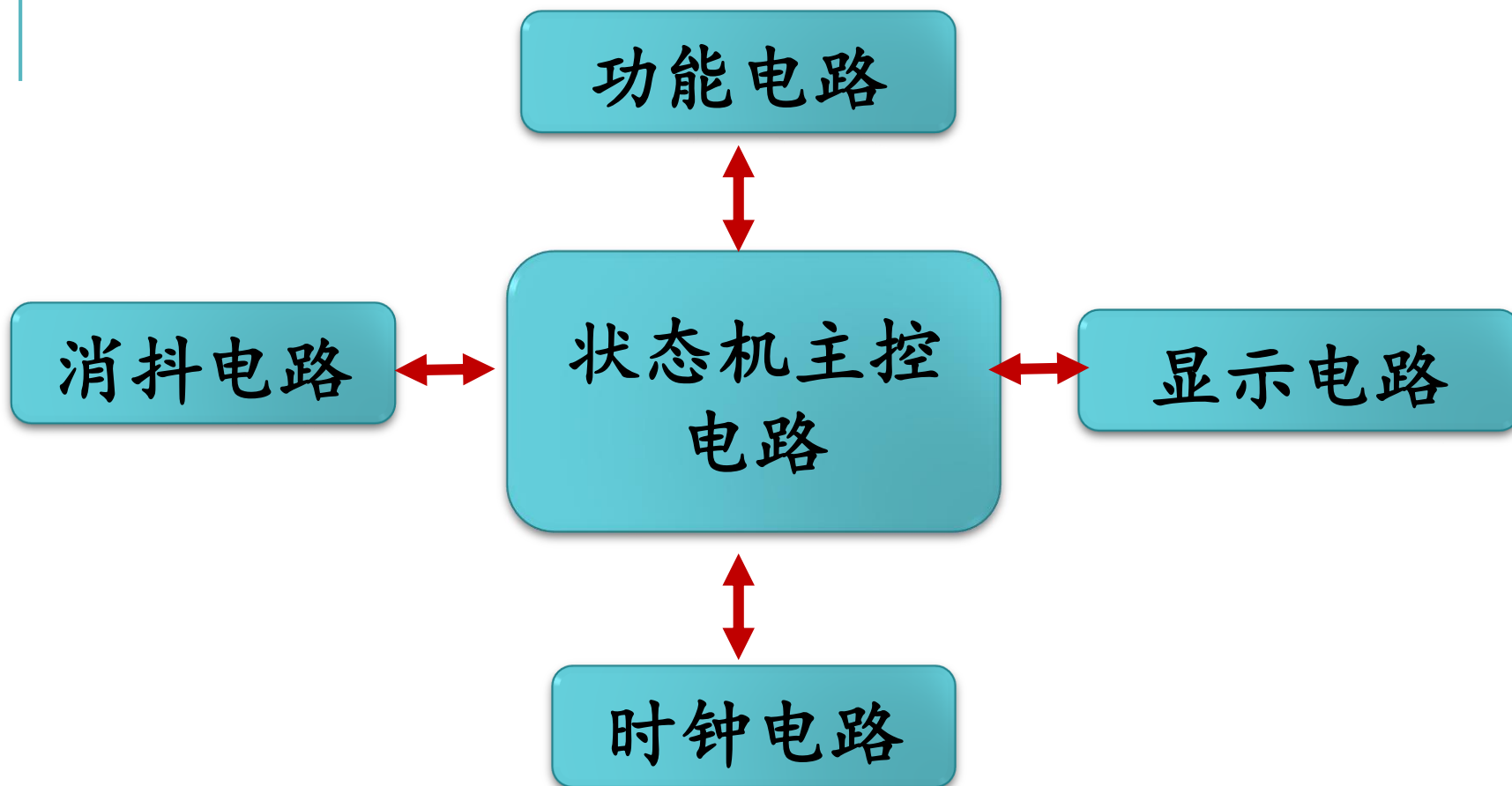实验板上有40MHz的时钟信号，对应FPGA引脚号为PIN_152，自动售货机的工作时钟及数码管循环扫描显示的时钟可由该40MHz分频得到。



消抖电路

  

```
// Switch Debounce Module
// use your system clock for the clock input
// to produce a synchronous, debounced output
// DELAY = .01 sec with a 27Mhz clock
module debounce #(parameter DELAY=270000-1)
    (input reset, clock, bouncey,
     output reg steady);
```

```
    reg [18:0] count;
    reg old;
```

```
    always @(posedge clock)
        if (reset) // return to known state
            begin
                count <= 0;
                old <= bouncey;
                steady <= bouncey;
            end
        else if (bouncey != old) // input changed
            begin
                old <= bouncey;
                count <= 0;
            end
        else if (count == DELAY) // stable!
            steady <= old;
        else // waiting...
            count <= count+1;
```

```
endmodule
```