

基于FPGA的 组合逻辑电路设计和实现 EDA实验一

赵晓燕
电工电子实验中心

主要内容

一、FPGA：PLD的最新发展

二、FPGA设计流程


三、HDL硬件描述语言

四、基于FPGA的组合逻辑电路实现

五、EDA实验一内容布置


六、EDA实验二内容展望

一、FPGA：PLD的最新发展

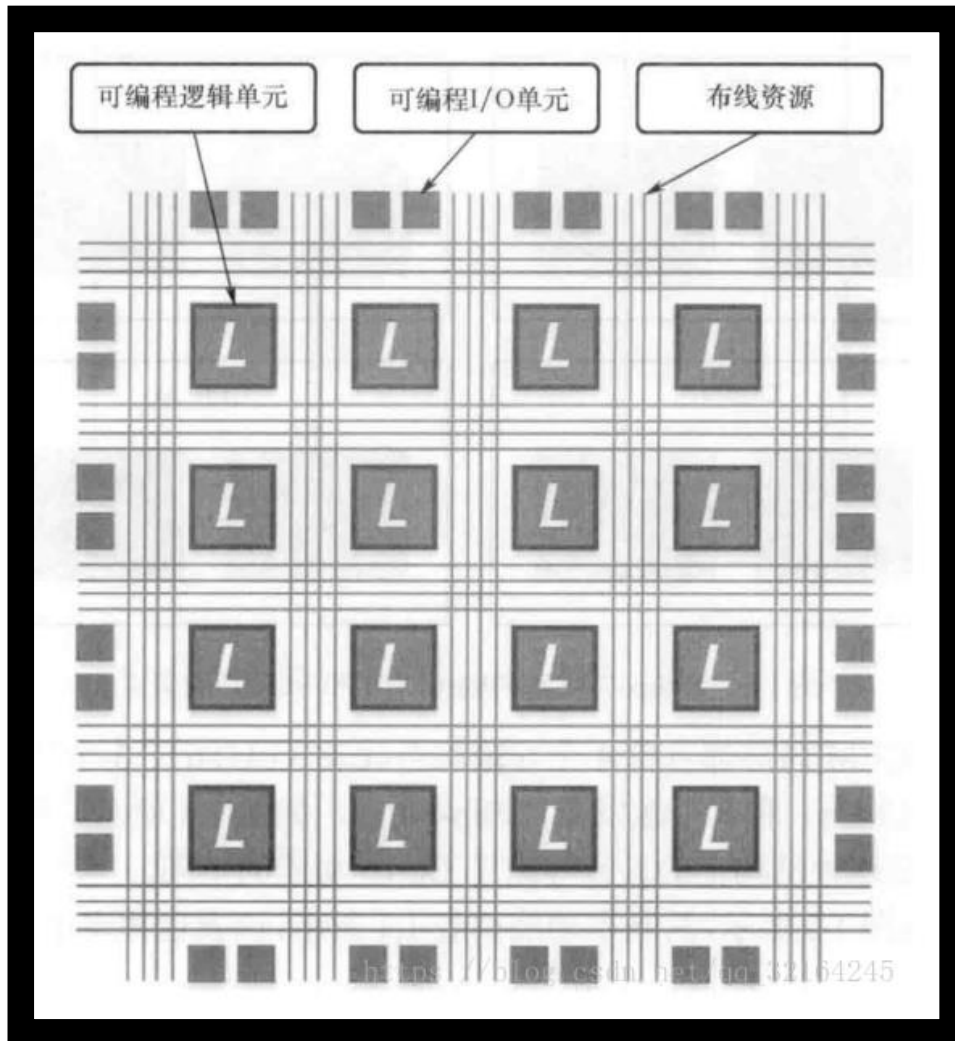


实验板FPGA芯片：
EP3C16Q240C8N

FPGA: Field Programmable Gate Array

 


An FPGA is like an electronic breadboard that is wired together by an automated **synthesis tool**

二、FPGA设计流程

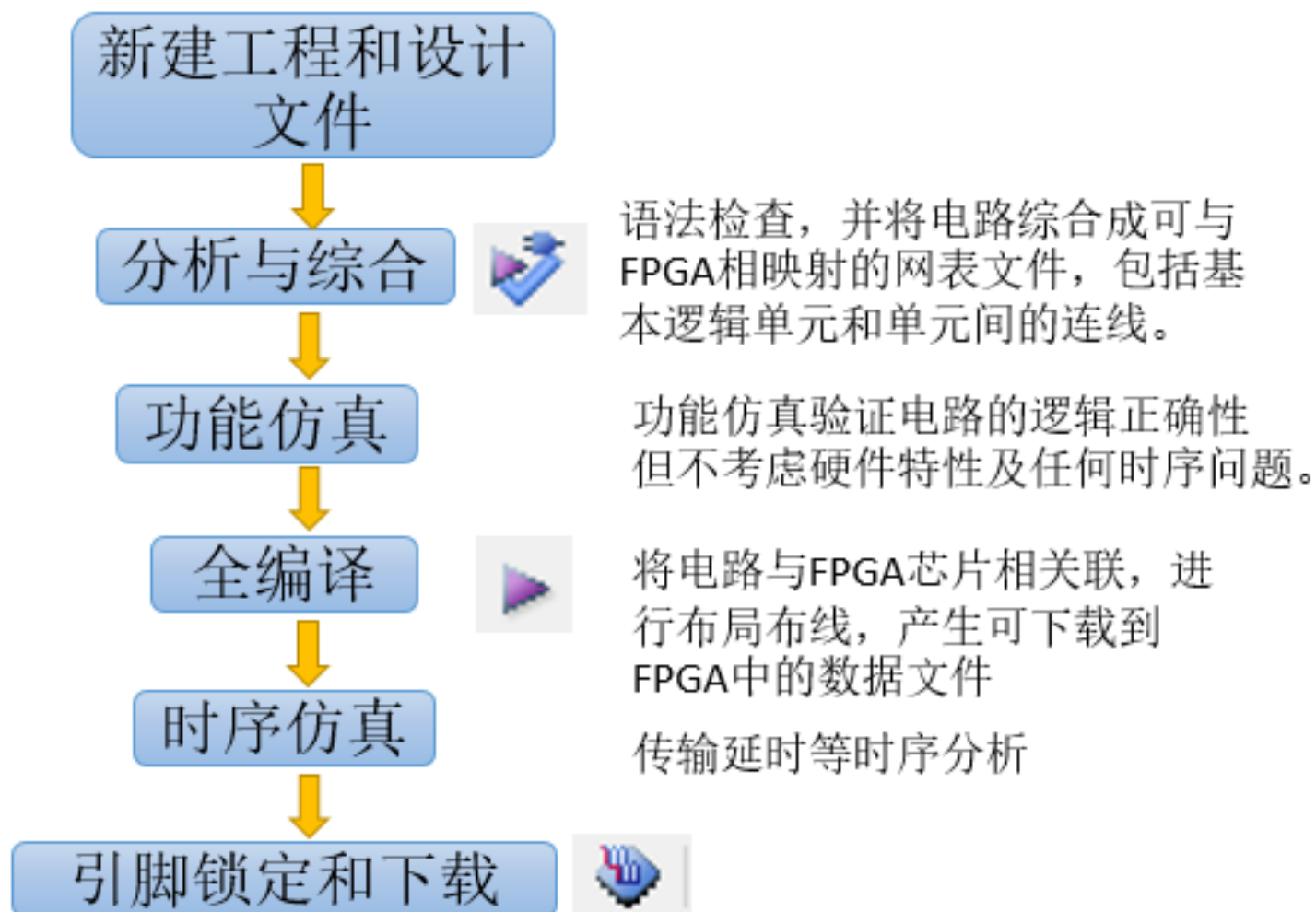

操作实例

 

$$y = ac' + bc$$

Quartus 13.0软件界面


工程路径

工程对象栏

主设计窗口

任务栏

信息栏

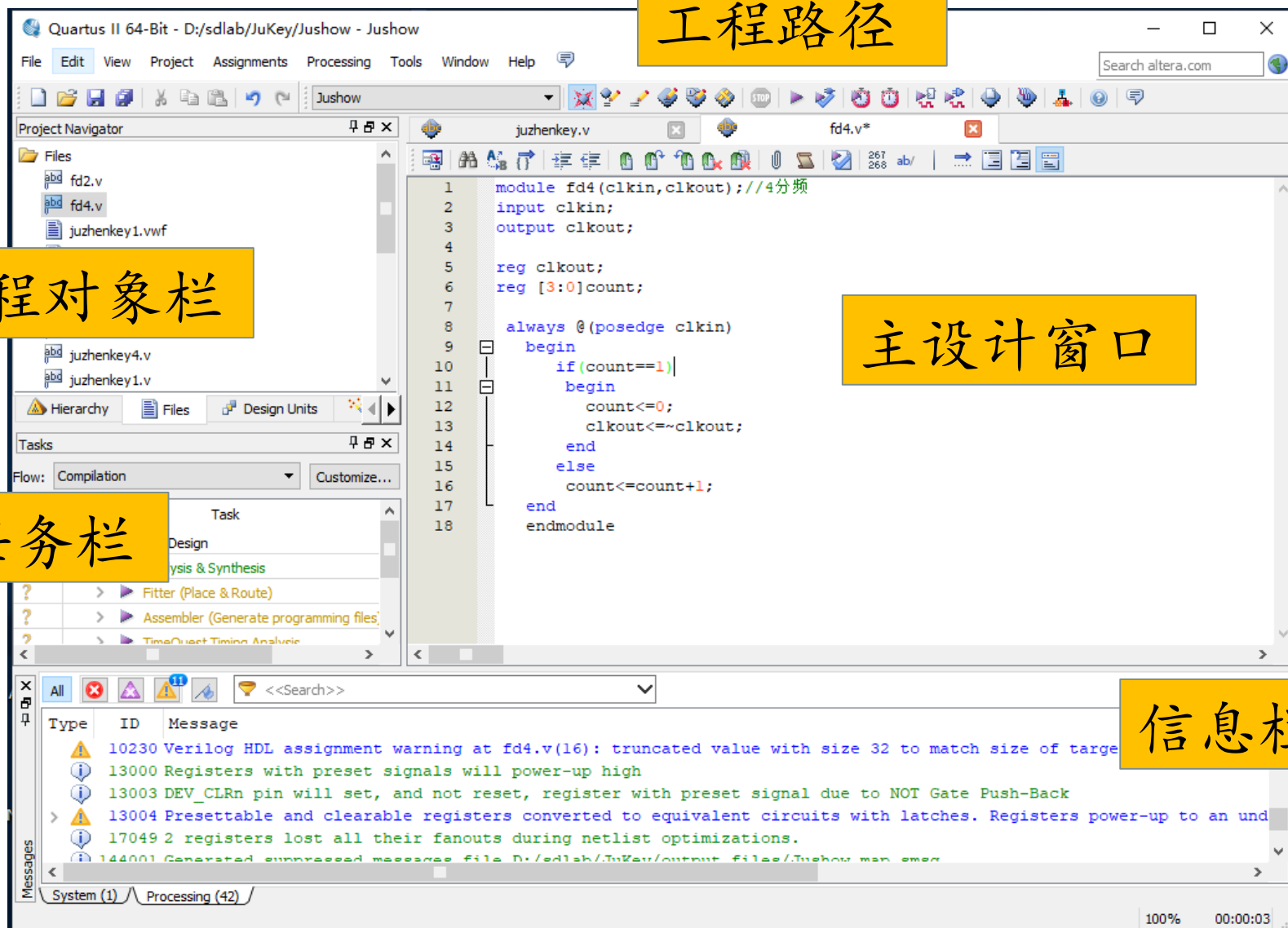


1、新建工程(*.qpf)

打开工程向导



创建工程目录路径
创建工程名
创建工程顶层实体名

注意：
路径名和工程名不要
有中文和空格

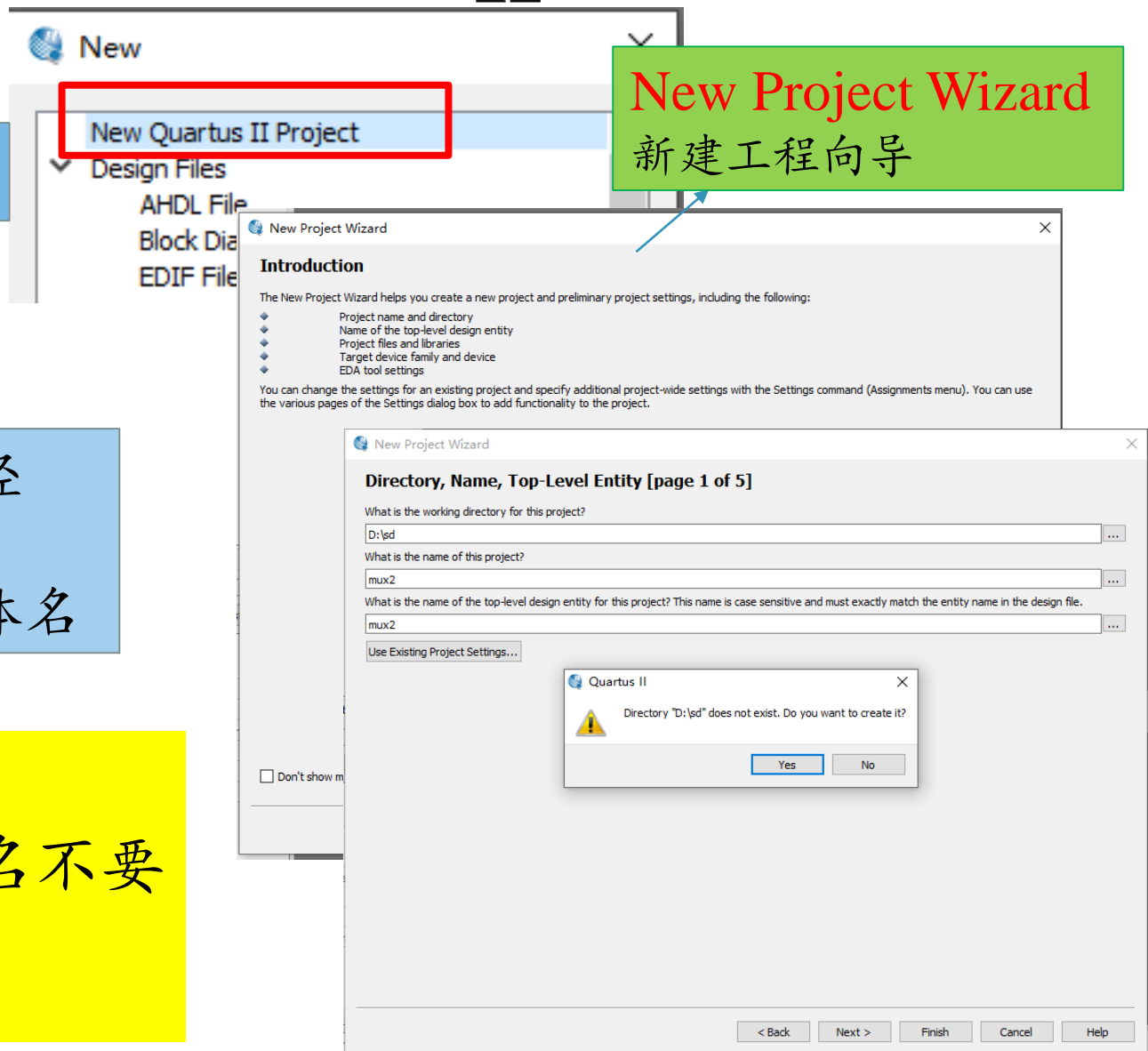


2、输入设计文件(*.bdf原理图文件)

打开原理图编辑器




绘制原理图


放置器件

 

放置连线

 


放置输入、
输出口

 


定义输入、输出口

New

×

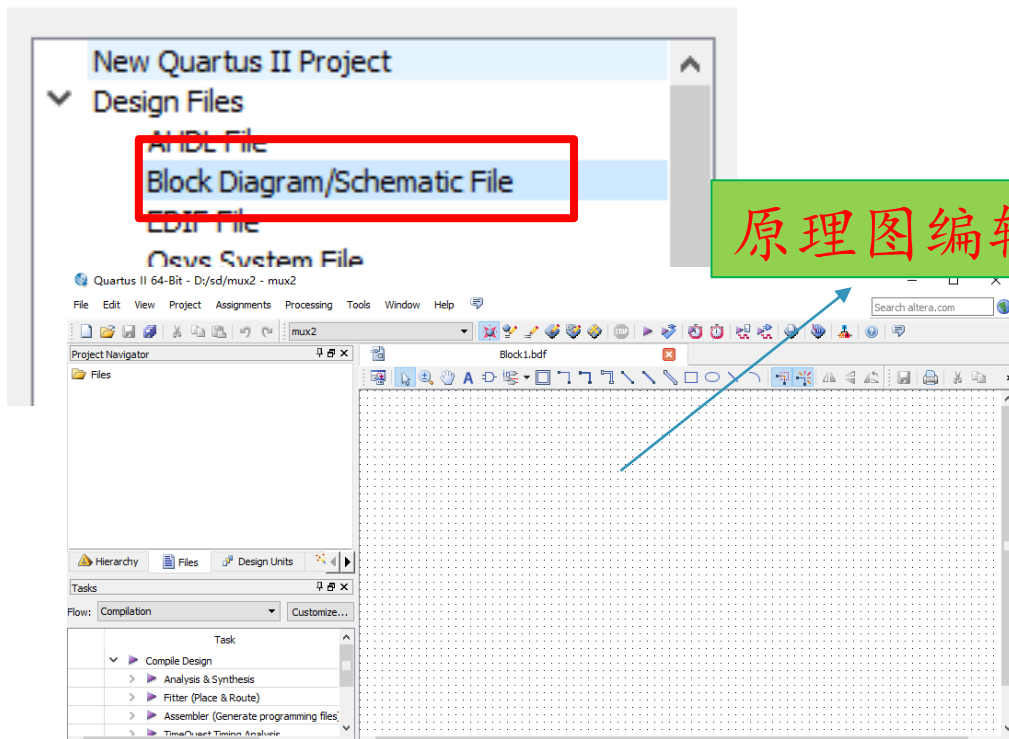

原理图编辑器

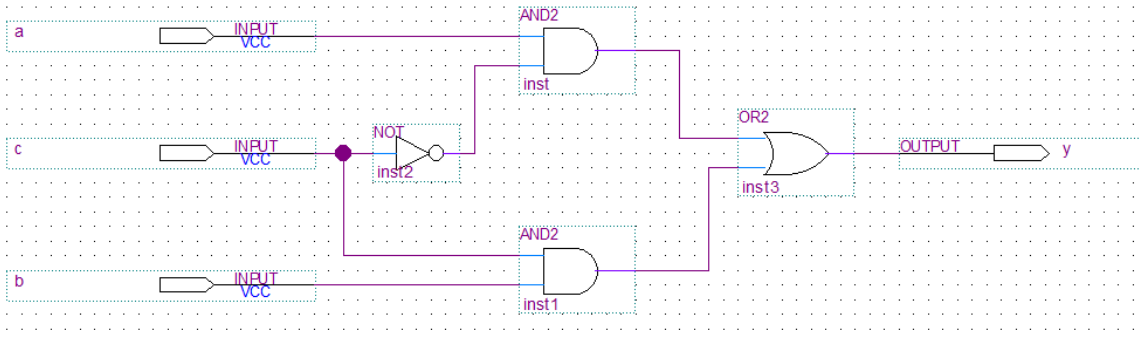


3、综合与分析



将被仿真文件置顶






综合与分析

 

■ 软件自动完成综合

■ 注意信息栏修改错误

 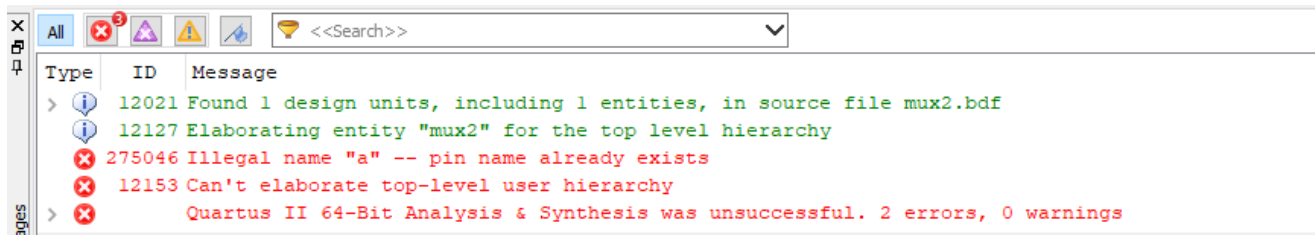 


错误，可检查语法问题、不能检查算法问题（仿真波形，RTL Viewer）



警告，综合分析没问题，全编译会有问题

4、功能仿真 (*.vwf波形文件)

 

波形编辑器

打开波形编辑器

导入信号节点





设置仿真信号

选择仿真器



注意：
仿真执行的前提：


- 被仿真文件置顶
- 综合分析无错误

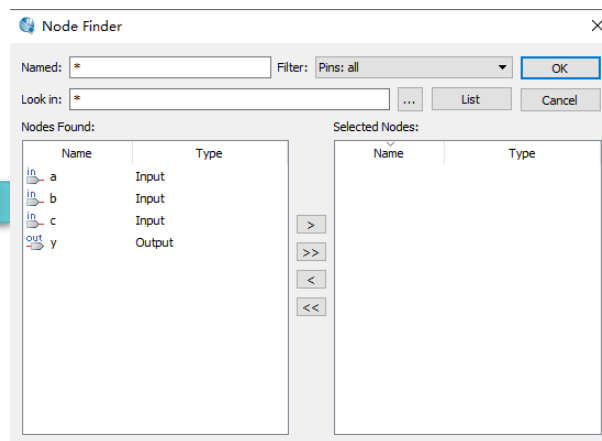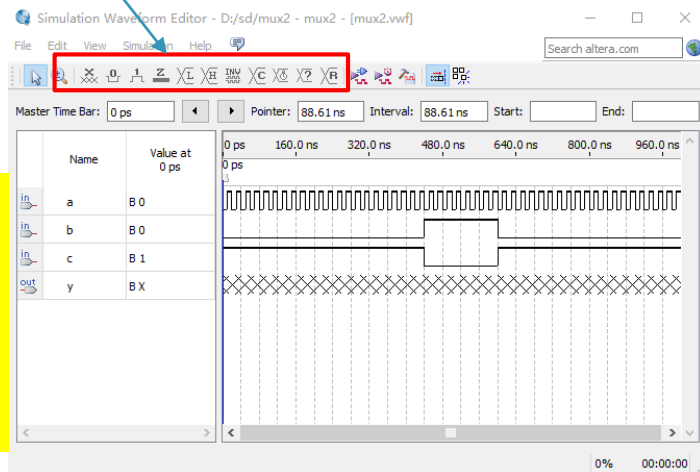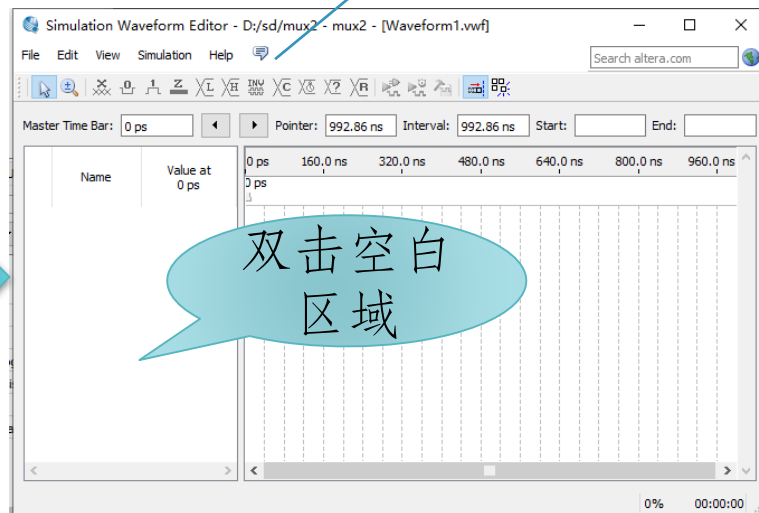 


逻辑功能验证

$$y = ac' + bc$$

仿真波形可检验逻辑设计的正确与否（调试）

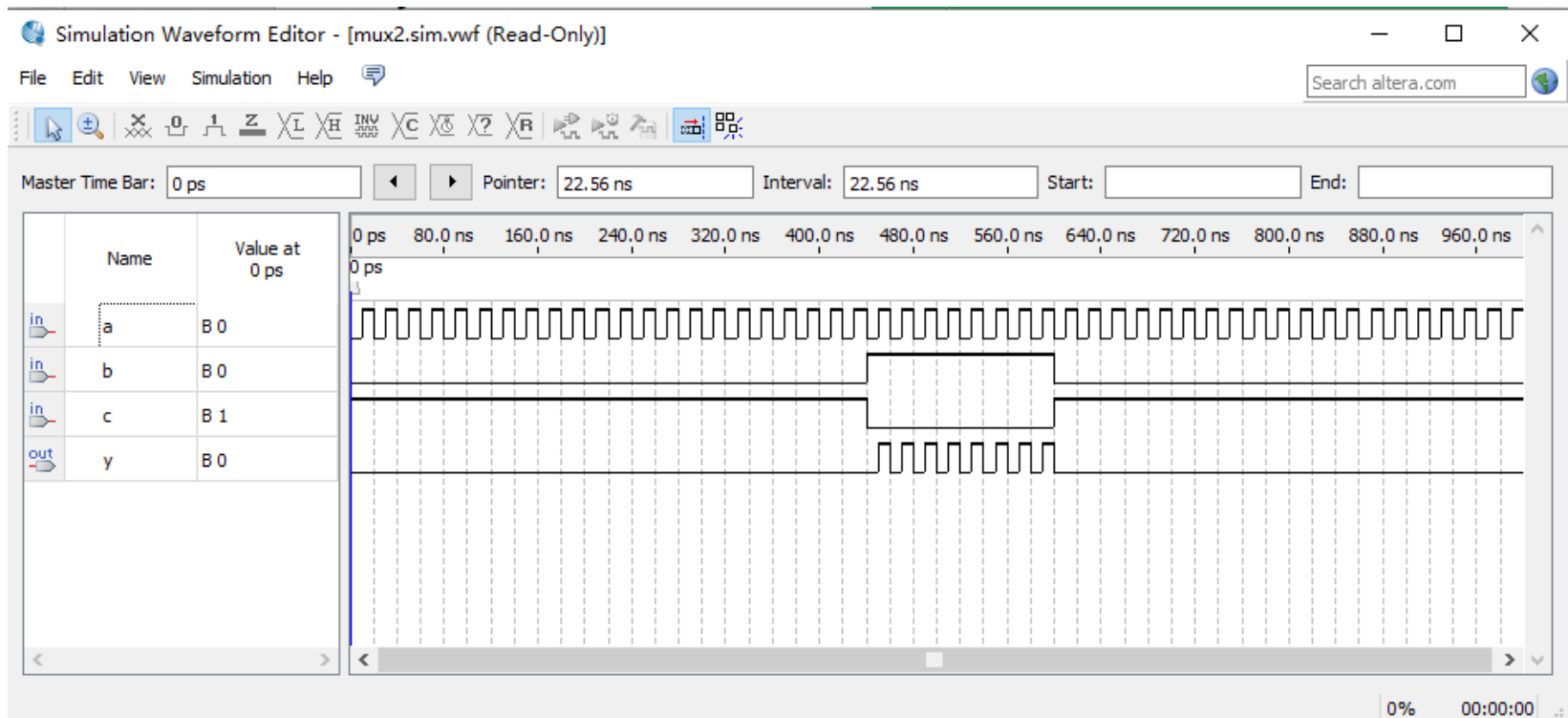

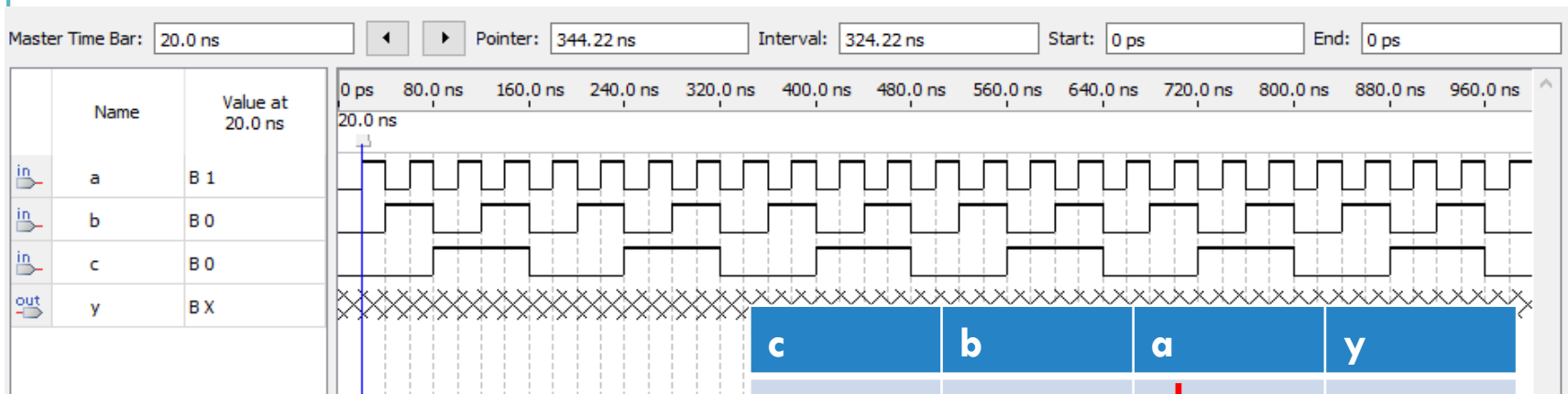

仿真波形设置要遍历
输入所有可能情况

c	b	a	y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

5、时序仿真（可选）

全编译



时序仿真



6、引脚锁定和下载



引脚分配



全编译



下载

 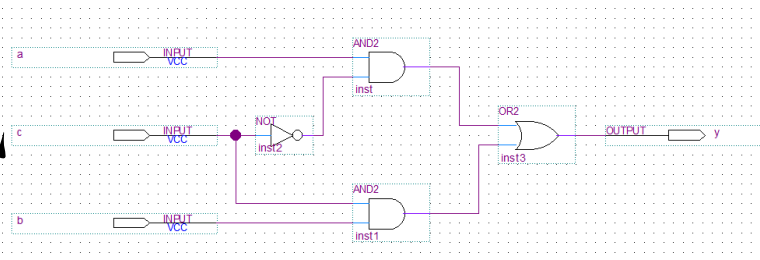

LED3	LED4	LED5	LED6
PIN_145	PIN_146	PIN_167	PIN_168

输入为 1 时，相应的发光二极管被点亮

SW1	SW2	SW3	SW4	SW5	SW6	SW7	SW8
PIN_160	PIN_161	PIN_166	PIN_164	PIN_174	PIN_175	PIN_177	PIN_176

开关在上端输出0，开关在下端输出1

Named: * Edit: [X] [Y]		
Node Name	Direction	Location
in a	Input	PIN_160
in b	Input	PIN_161
in c	Input	PIN_166
out y	Output	PIN_146

Assignments	Processing	Tools	Win
Device...			
Pins			
Timing Analysis Settings...			
EDA Tool Settings...			
Settings...			Ctrl+Shift+E


设计文件输入

➤ 原理图输入

➤ 代码（HDL）输入


➤ 混合输入


原理图输入 (以一位全加器为例)

 


封装




Open	
Remove File from Project	
 Set as Top-Level Entity	Ctrl+Shift+J
Create AHDL Include Files for Current File	
Create Symbol Files for Current File	
Properties...	

 



add1

 

代码 (HDL) 输入

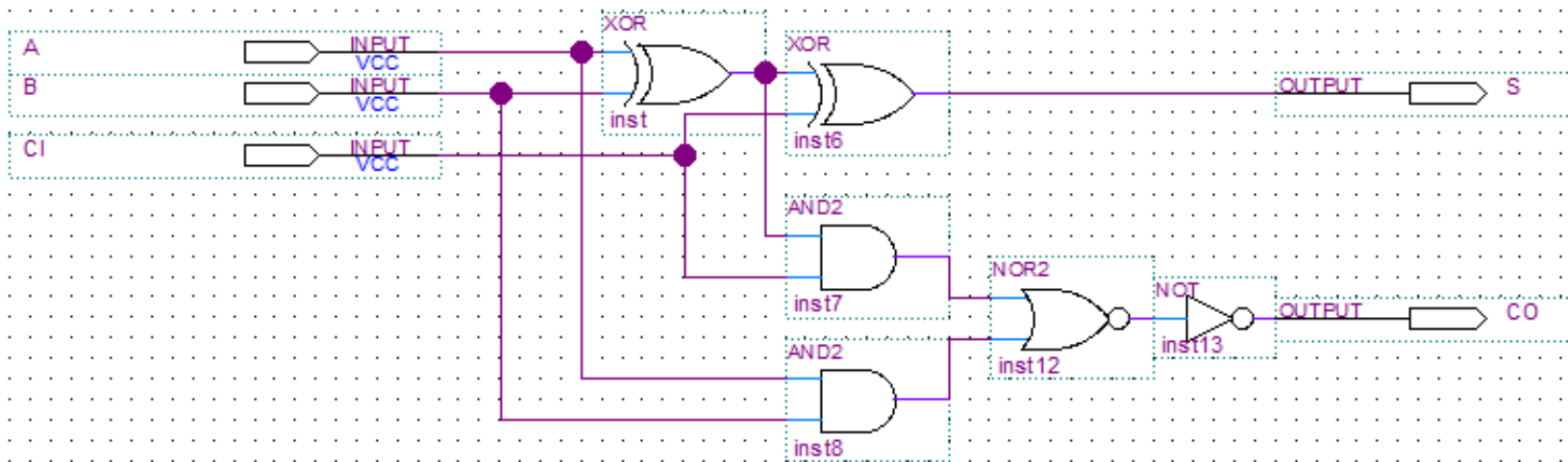

或者：HDL输入

  

```
module add1(a,b,ci,s,co);
```


```
input a,b,ci;
```

```
output s,co;
```

```
assign {co, s} = a + b + ci;
```

```
endmodule
```

混合输入

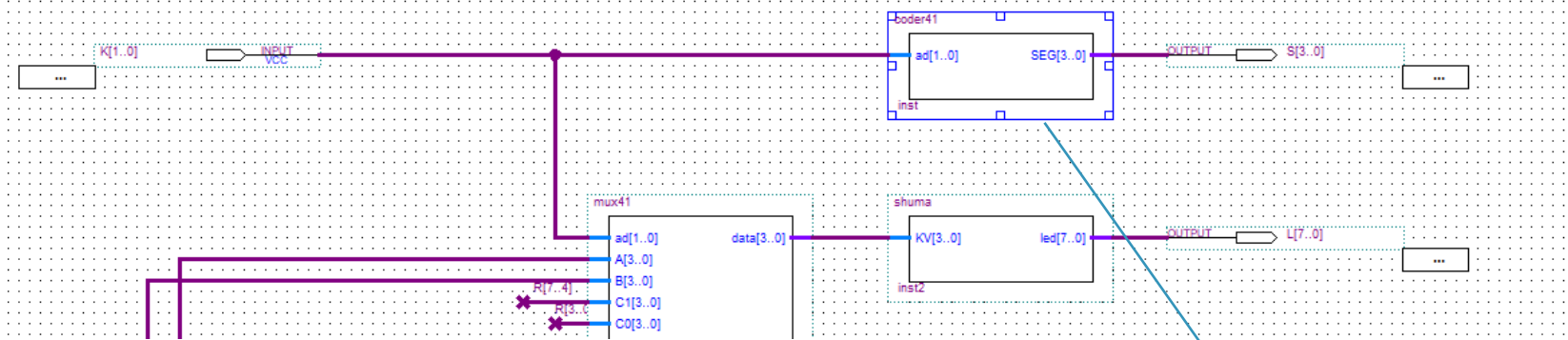

- 电路信号关系直观明确
- 顶层模块原理图输入
- 底层模块代码输入

```
1 module coder41(ad,SEG);
2   input[1:0] ad;
3   output[3:0]SEG;
4   reg [3:0]SEG;
5
6   always@(*)
7   case(ad)
8     2'b00: SEG=4'b0111;
9     2'b01: SEG=4'b1011;
10    2'b10: SEG=4'b1101;
11    2'b11: SEG=4'b1110;
12
13  endcase
14 endmodule
```

三、硬件描述语言HDL

- A high-level programming language offering special constructs to model microelectronic circuits
 - Describe the operation of a circuit at various level of abstraction
 - Behavior
 - Function
 - Structure
 - Describe the timing of a circuit
 - Express the concurrency of circuit operation
 - Similar to C
- Trend
 - Designers think in functionality
 - CAD tools take care of implementation

Verilog HDL vs. VHDL

- Verilog HDL结构比较灵活，是一种非常容易掌握的硬件描述语言（类C语言）。
- VHDL语言的高层抽象能力要稍优一些。语言规范十分严谨，甚至于繁琐，但是可读性却十分好。
- 大学、研究机构更多使用VHDL，而工业界更多使用Verilog HDL。

Hardware structures can be modeled effectively in either VHDL and Verilog. Verilog is similar to c and a bit easier to learn.

VHDL(Very High Speed Integrated Circuit Hardware Description Language)

Verilog HDL与VHDL描述加法器电路

library ieee;	
Use ieee.std_logic_1164.all;	
Use ieee.std_logic_arith.all;	
entity vadd is	module kadd (a,b,c,s);
port (a,b: in std_logic_vector(7 downto 0);	input[7:0] a ,b;
c: in std_logic_vector(0 to 0);	input c;
s : out std_logic_vector(8 downto 0));	output[8:0] s;
End vadd;	
architecture rtl of vadd is	
begin	
s <= unsigned(a)+unsigned(b)+unsigned(c);	assign s = a+b+c;
End rtl;	endmodule


Verilog与C语言

C	Verilog
sub-function	module、function、task
if、else if、else	if、else if、else
case	case
{}	begin、end
for	for
while	while
break	disable
define	define
int	int
printf	monitor、display、strobe

C	Verilog	功 能
>=	>=	大于等于
<=	<=	小于等于
==	==	等于
!=	!=	不等于
~	~	位反相
&	&	按位逻辑与
		按位逻辑或

C	Verilog	功 能
*	*	乘
/	/	除
+	+	加
-	-	减
%	%	取模
!	!	反逻辑
&&	&&	逻辑与
		逻辑或
>	>	大于
<	<	小于

代码描述方式

 

➤ 结构描述（画电路）

➤ 数据流描述（写逻辑函数表达式）

➤ 行为描述

Dataflow Description

- Verilog designs consist of interconnected **modules**.
- A module can be an element or collection of lower level design blocks.
- A simple module with combinational logic might look like this:

定义外部接口


```
module mux_2_to_1(a, b, out,  
                  outbar, sel);
```

```
// This is 2:1 multiplexor
```

```
input a, b, sel;  
output out, outbar;
```

```
assign out = sel ? a : b;  
assign outbar = ~out;
```

```
endmodule
```

 

$$\text{Out} = \text{sel} \bullet a + \text{sel}' \bullet b$$

2-to-1 multiplexer with inverted output

Declare and name a module; list its ports. Don't forget that semicolon.

Comment starts with //
Verilog skips from // to end of the line


Specify each port as input, output, or inout

Express the module's behavior. Each statement executes in parallel; order does not matter.

Conclude the module code.

Structure Description
 
```
module muxgate (a, b, out,  
outbar, sel);  
input a, b, sel;  
output out, outbar;  
wire out1, out2, selb;  
and a1 (out1, a, sel);  
not i1 (selb, sel);  
and a2 (out2, b, selb);  
or o1 (out, out1, out2);  
assign outbar = ~out;  
endmodule
```



- Verilog supports basic logic gates as primitives
 - and, nand, or, nor, xor, xnor, not, buf
 - can be extended to multiple inputs: e.g., nand nand3in (out, in1, in2,in3);
 - bufif1 and bufif0 are tri-state buffers
- Net represents connections between hardware elements. Nets are declared with the keyword `wire`.

Behavior Description

- Procedural assignment allows an alternative, often higher-level, behavioral description of combinational logic
- Two structured procedure statements: `initial` and `always`
- Supports richer, C-like control structures such as `if`, `for`, `while`, `case`

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;
```

Exactly the same as before.

```
    reg out, outbar;
```

Anything assigned in an `always` block must *also* be declared as type `reg`

```
    always @ (a or b or sel)
```

Conceptually, the `always` block runs whenever a signal in the **sensitivity list** changes value

```
    begin
```

```
        if (sel) out = a;  
        else out = b;
```

```
        outbar = ~out;
```

Statements within the `always` block are executed sequentially. Order matters!

```
    end
```

Surround multiple statements in a single `always` block with `begin/end`.

```
endmodule
```

The case Statement

- case and if may be used interchangeably to implement conditional execution within always blocks
- case is easier to read than a long string of if...else statements

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;  
    reg out;  
  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end  
  
    assign outbar = ~out;  
  
endmodule
```

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;  
    reg out;  
  
    always @ (a or b or sel)  
    begin  
        case (sel)  
            1'b1: out = a;  
            1'b0: out = b;  
        endcase  
    end  
  
    assign outbar = ~out;  
  
endmodule
```

*Note: Number specification notation: <size>'<base><number>
(4'b1010 if a 4-bit binary value, 16'h6cda is a 16 bit hex number, and 8'd40 is an 8-bit decimal value)*

Module Structure

```
module M (P1, P2, P3, P4);  
    input P1, P2;  
    output [7:0] P3;  
    inout P4;
```

```
    reg [7:0] R1, M1[1:1024];  
    wire W1, W2, W3, W4;  
    parameter C1 = "This is a string";
```

```
    initial  
    begin : BlockName  
        // Statements  
    end
```

```
    always  
    begin  
        // Statements  
    end
```

```
    // Continuous assignments...  
    assign W1 = Expression;
```

```
    // Module instances...  
    COMP U1 (W3, W4);  
    COMP U2 (.P1(W3), .P2(W4));
```


```
endmodule
```

代码结构

- 端口定义
- 变量定义
- 并行执行语句
 - 过程语句
 - 连续赋值语句
 - 模块实例化语句
- 顺序执行语句


调试

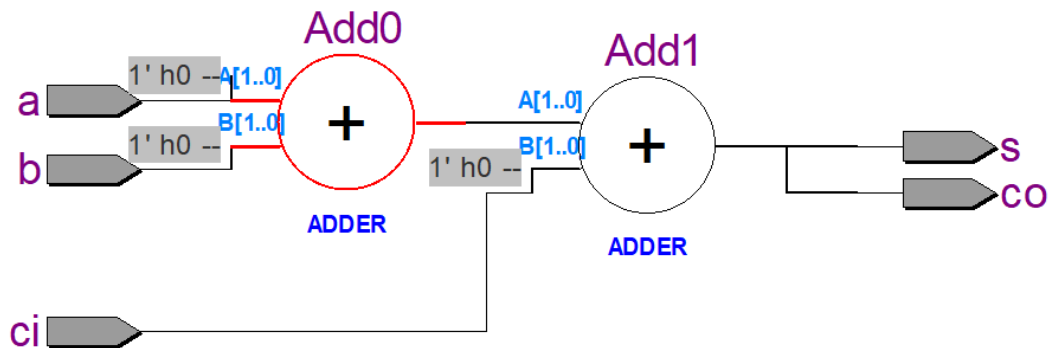- 功能或时序仿真(Modelsim或quartus波形文件或测试文件)
- 利用板子外设、信号发生器、示波器
- RTL Viewer



Tools->Netlist Viewers->RTL Viewer


四、基于FPGA的组合逻辑电路实现

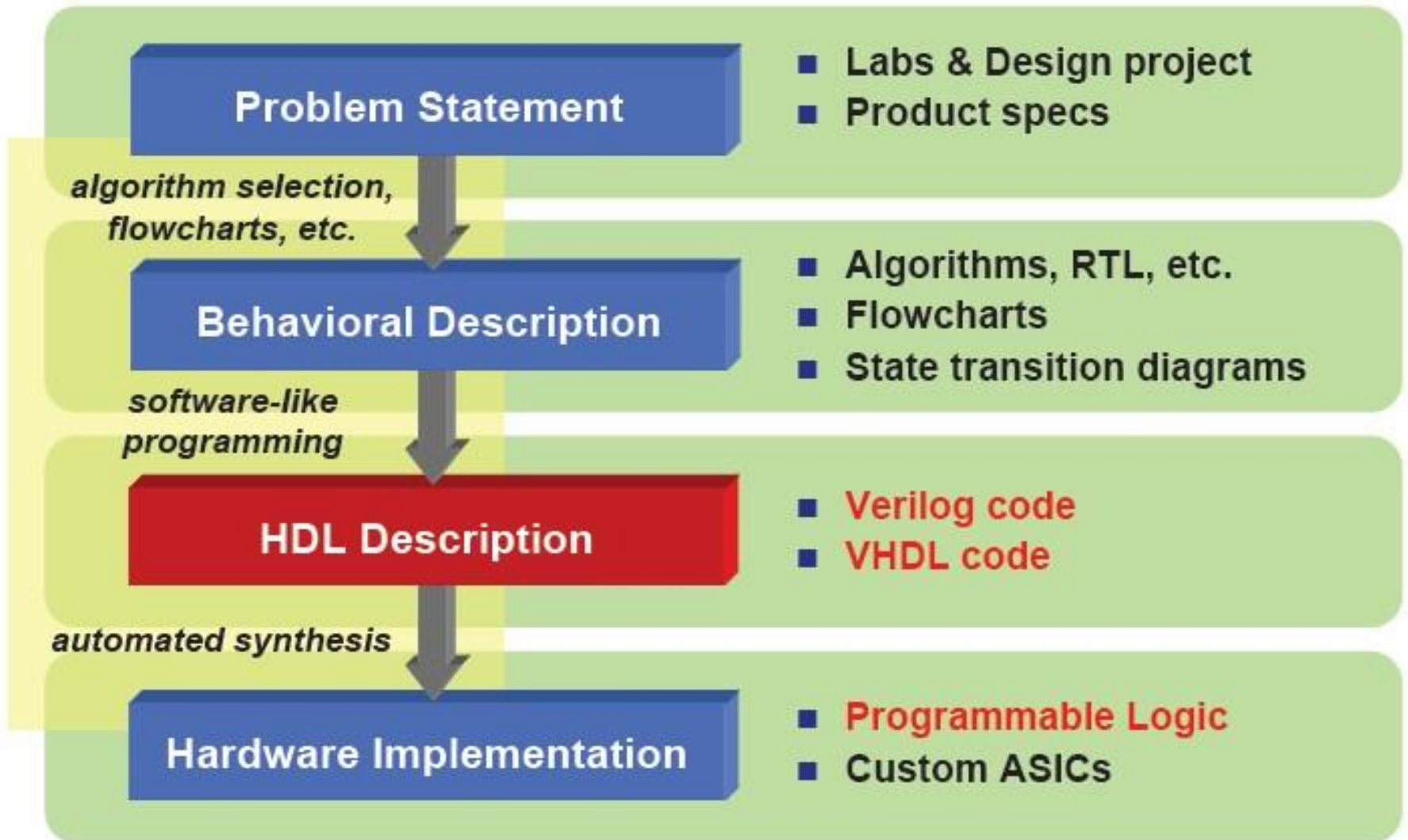

自顶向下的设计

- Modularity is essential to the success of large designs
- A Verilog module may contain submodules that are “wired together”
- High-level primitives enable direct synthesis of behavioral descriptions (functions such as additions, subtractions, shifts (<< and >>), etc.

Example: A 32-bit ALU

 

Function Table

F2	F1	F0	Function
0	0	0	$A + B$
0	0	1	$A + 1$
0	1	0	$A - B$
0	1	1	$A - 1$
1	0	X	$A * B$

自底向上的实现

2-to-1 MUX

```
module mux32two(i0,i1,sel,out);
input [31:0] i0,i1;
input sel;
output [31:0] out;

assign out = sel ? i1 : i0;

endmodule
```

3-to-1 MUX

```
module mux32three(i0,i1,i2,sel,out);
input [31:0] i0,i1,i2;
input [1:0] sel;
output [31:0] out;
reg [31:0] out;

always @ (i0 or i1 or i2 or sel)
begin
    case (sel)
        2'b00: out = i0;
        2'b01: out = i1;
        2'b10: out = i2;
        default: out = 32'bx;
    endcase
end
endmodule
```

32-bit Adder

```
module add32(i0,i1,sum);
input [31:0] i0,i1;
output [31:0] sum;

assign sum = i0 + i1;

endmodule
```

32-bit Subtractor

```
module sub32(i0,i1,diff);
input [31:0] i0,i1;
output [31:0] diff;

assign diff = i0 - i1;

endmodule
```

16-bit Multiplier

```
module mul16(i0,i1,prod);
input [15:0] i0,i1;
output [31:0] prod;

// this is a magnitude multiplier
// signed arithmetic later
assign prod = i0 * i1;

endmodule
```

自底向上的实现

■ Given submodules:

```
module mux32two(i0,i1,sel,out);
module mux32three(i0,i1,i2,sel,out);
module add32(i0,i1,sum);
module sub32(i0,i1,diff);
module mul16(i0,i1,prod);
```

■ Declaration of the ALU Module:

```
module alu(a, b, f, r);
  input [31:0] a, b;
  input [2:0] f;
  output [31:0] r;
```

```
  wire [31:0] addmux_out, submux_out;
  wire [31:0] add_out, sub_out, mul_out;
```


```
  mux32two    adder_mux(b, 32'b1, f[0], addmux_out);
  mux32two    sub_mux(b, 32'b1, f[0], submux_out);
  add32       our_adder(a, addmux_out, add_out);
  sub32       our_subtractor(a, submux_out, sub_out);
  mul16       our_multiplier(a[15:0], b[15:0], mul_out);
  mux32three  output_mux(add_out, sub_out, mul_out, f[2:1], r);
```

endmodule

module
names

(unique)
instance
names


corresponding
wires/regs in
module alu

 

五、EDA实验一内容布置

基本内容

基于FPGA实现一个简易计算器：

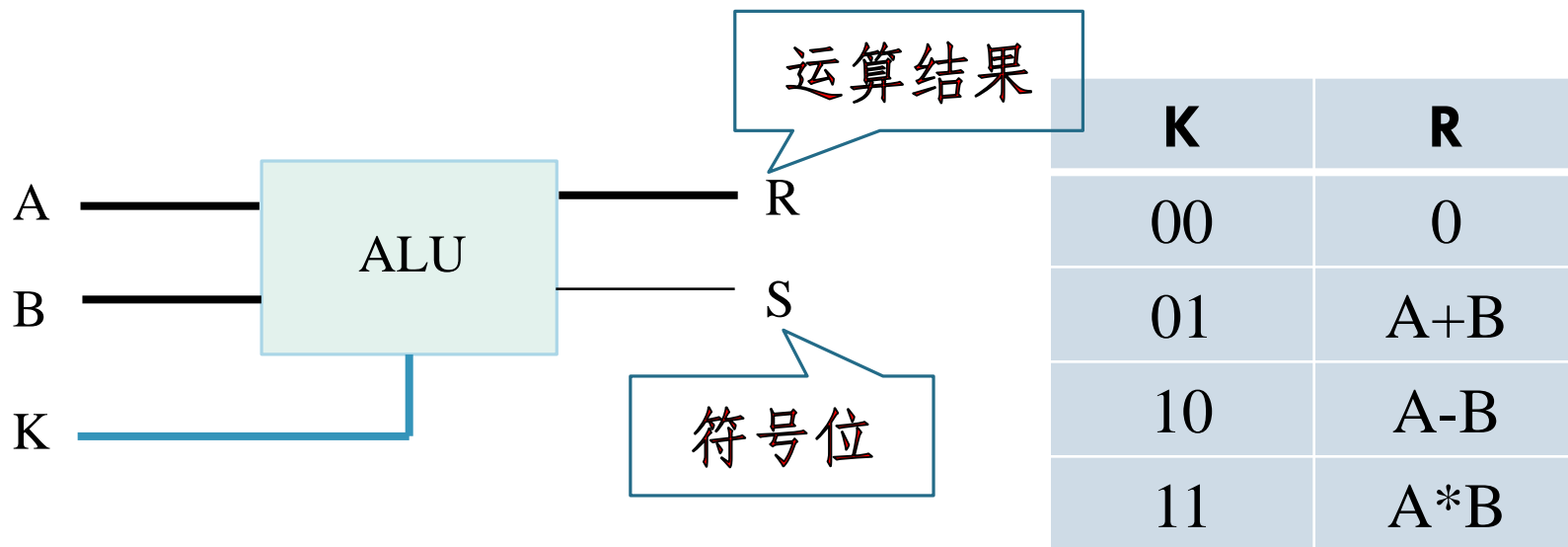


其中A和B的取值范围为0~15；用实验板上的拨码开关和按键开关模拟输入；在数码管上以十六进制形式显示运算数和运算结果，负号用发光二极管显示。


数码管

按键
开关

发光二极管



拨码开关

 

 

EDA实验一中用两个按键开关控制数码管的显示

EDA实验二中将学习循环扫描显示

  

六、EDA实验二内容展望

Vending machine



利用实验板上的拨码开关和按键开关模拟**投币**、**购物**和**退币**输入，用**发光二极管**模拟各种提示信息，用**数码管**显示余额，实现一个自动售货机内部控制电路。要求满足如下规格：

- 1) 可接受**5角**、**1元**和**5元**的投币，每次购买允许投入多种不同币值的钱币；用**3只数码管**显示当前投币金额，如055表示已投币5.5元；
- 2) 可售出价格分别为**1.5元**和**2.5元**的商品，假设用户每次购买时只选择单件、一种商品；允许用户多次购买商品，每次购买后，可以进行补充投币；
- 3) 选择购买商品后，如果投币**金额不足**，则提醒；否则，售出相应的商品，并提醒用户取走商品；
- 4) 若用户选择**退币**，则退回余下的钱，并提醒用户取钱。